

## Figures for EET-200 Exam #1.

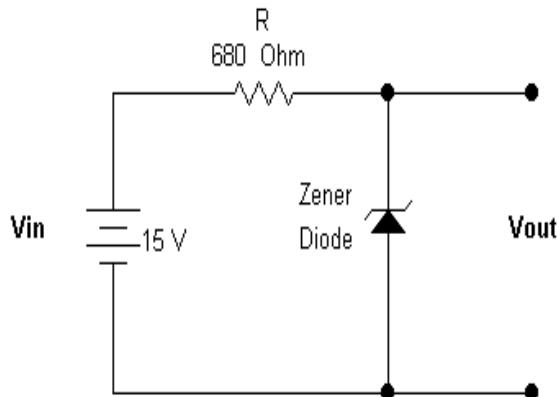


Fig. 1

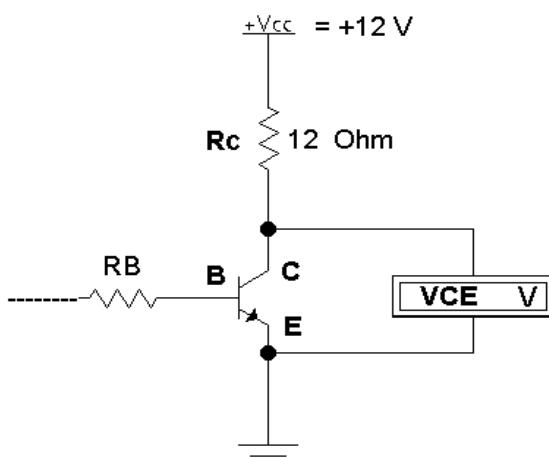


Fig. 2 NPN Transistor

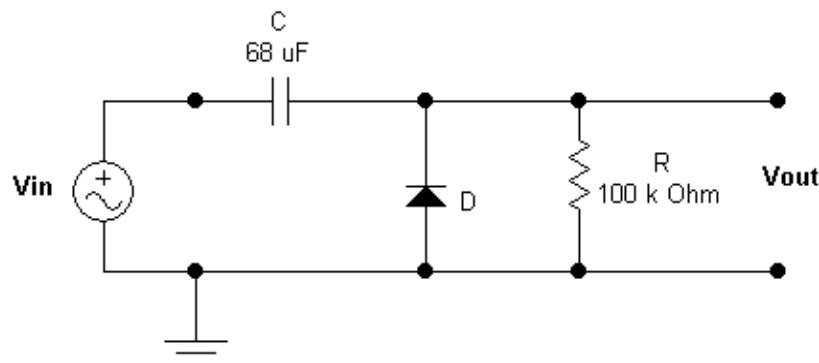


Fig. 3

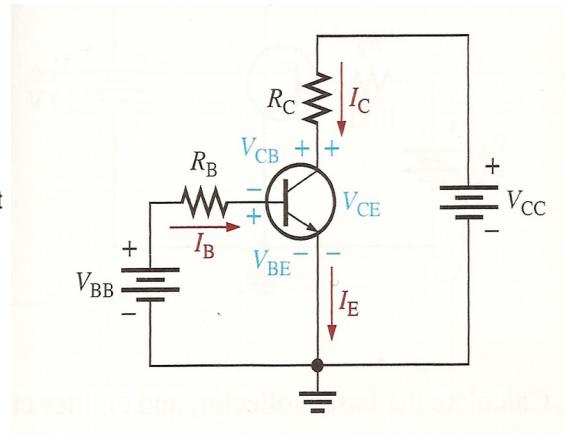


Fig. 4

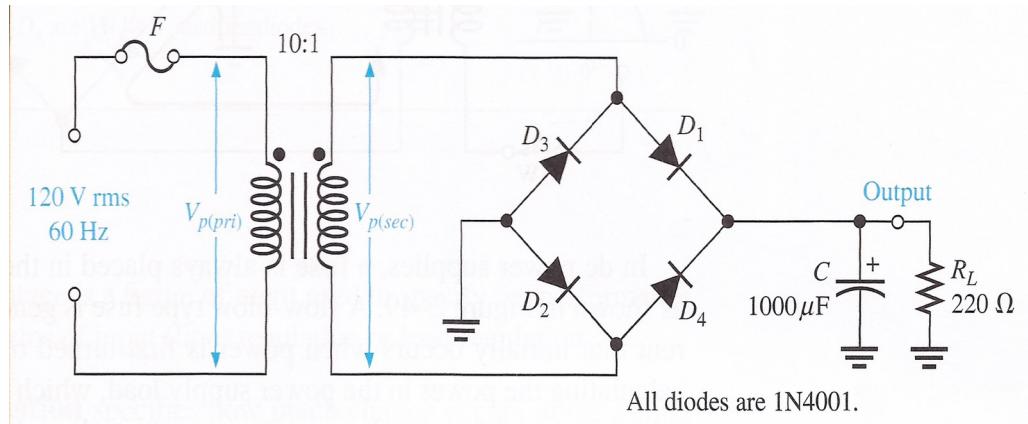


Fig. 5

(Fig. 6 on other side)

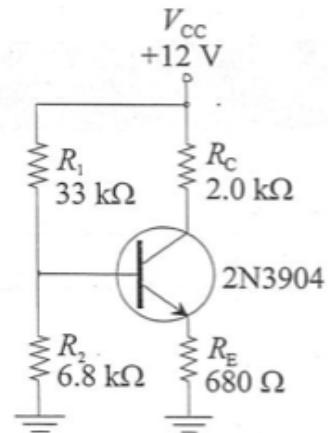


Figure 5-3

**Fig. 6.** (From Lab on Transistor Biasing)