

- 1) Determine the voltage, current and power gain, as a ratio and in dBs, of an amplifier with the following input/output characteristics:

$$V_{in} = 25 \text{ mV}$$

$$V_{out} = 4.4 \text{ V}$$

$$I_{in} = 600 \text{ } \mu\text{A}$$

$$I_{out} = 85 \text{ mA}$$

- 2) An amplifier has a +30 dB voltage gain and an input voltage of 1 mV. Determine the output voltage (in volts).
- 3) A 5 Vp 400 MHz signal is input into 500 feet of cable (RG-6/U) which has an attenuation of -4 dB/100 feet. Determine the gain of the repeater (amplifier) needed at the end of this cable so that:
- The signal is restored to 5 Vp.
 - The signal is increased to 10 Vp.
- 4) A student makes the following measurements on a differential amplifier using a 500 mVp input source:
- $V_{out (DM)}$ = Differential Mode Output Voltage = 10 Vp
 $V_{out (CM)}$ = Common Mode Output Voltage = 75 μ Vp
- Determine the Differential Mode Gain as a ratio & in dBs.
 - Determine the Common Mode Gain as a ratio & in dBs.
 - Determine the Common Mode Rejection Ratio (CMRR) as a ratio and in dBs.
- 5) A differential amplifier has an input consisting of 10 mVp of 250 Hz signal and 100mVp of 60 Hz noise. The amplifier has a differential gain of +40 dB with a C.M.R.R. of +71.5 dB. Determine the following:
- The input S/N ratio. (This is the signal to noise ratio, it is the ratio of the signal voltage to the noise voltage.) Express this as a ratio and in dB. (Hint: $S/N = 0.1$ as a ratio for the input.)
 - The differential and common mode gains expressed in dB and ratio form. (Hint: $A_{CM} = -31.5 \text{ dB}$)
 - The signal and noise amplitudes at the output of the amplifier.
 - The S/N ratio at the output of the amplifier expressed as a ratio and in dB. (Hint: $S/N = +51.5 \text{ dB}$)
 - Studying your answers for part a. and part d., How could the output S/N ratio (in dB's) be easily determined knowing the input S/N and the C.M.R.R.?
- 6) An instrumentation amplifier (an improvement over the differential amplifier) has a C.M.R.R. of +120 dB. The input of this amplifier is a 50 μ Vp signal swamped with 1.5 Vp of noise (this corresponds to a -89.5 dB Signal-to-Noise ratio). If the differential gain of the instrumentation amplifier is +30 dB, determine:
- The common mode gain of the amplifier in dB.
 - The peak voltages of the signal and noise at the output of the amplifier.
 - The S/N ratio at the output in dBs.